

KNOWLEDGE PROBE 5: INTRODUCTION TO WIRELESS TECHNOLOGY

The Electronics of Wireless

Learning Objectives

1. Identify terms associated with wireless communication.
2. Distinguish between different types of receivers.
 1. A receiver that converts the incoming signal down to a lower frequency is called a
 - a. Dynamotor
 - b. Homodyne
 - c. Superheterodyne
 - d. Synchrodyne
 2. What circuit converts the incoming signal down to an IF?
 - a. Demodulator
 - b. LNA
 - c. Local oscillator
 - d. Mixer
 3. Why is the input signal downconverted?
 - a. Get rid of noise
 - b. Increase signal strength
 - c. Make tuning easier
 - d. Provide better selectivity
 4. A receiver has an incoming signal of 3.5 MHz. The local oscillator frequency is 3.955 MHz. What is the IF?
 - a. 455 kHz
 - b. 3.955 MHz
 - c. 7.455 MHz
 - d. 10.7 MHz
 5. In a receiver, if the received signal is digital, what circuit is used after demodulation to recover the original signal?
 - a. Analog-to-digital converter
 - b. Band pass filter
 - c. Demultiplexer
 - d. Digital-to-analog converter



6. Why is a LNA used in a receiver?
 - a. Amplify the very weak signal
 - b. Improve selectivity
 - c. Mitigate the noise
 - d. Mix the input with the LO signal
7. A radio the uses DSP for some signal processing is called a
 - a. Modulated receiver
 - b. Software-defined radio
 - c. Superheterodyne
 - d. Tuned radio frequency receiver
8. Which of the following is NOT usually preformed in a DSP?
 - a. Amplification
 - b. Demodulation
 - c. Filtering
 - d. Mixing
9. In a basic transmitter, the frequency of operation is set by
 - a. Dielectric resonator
 - b. LC resonant circuit
 - c. Quartz crystal
 - d. RC time constant
10. What signal source is used to select multiple frequencies in a transmitter?
 - a. Crystal oscillator
 - b. Frequency synthesizer
 - c. LC oscillator
 - d. RC oscillator
11. A mixer can be used for upconversion as well a downconversion.
 - a. True
 - b. False
12. What is the final stage of a transmitter that drives the antenna?
 - a. Frequency synthesizer
 - b. LNA
 - c. Modulator
 - d. Power amplifier
13. What usually controls the frequency synthesizer in a transmitter?
 - a. Flip flop
 - b. Embedded microcontroller
 - c. Crystal oscillator
 - d. Modulator



14. To use DSP in a transmitter or receiver, it must first be preceded by a(n)
- a. Analog-to-digital converter
 - b. Band pass filter.
 - c. Digital-to-analog converter
 - d. Power amplifier